

HINTS & TIPS

KIRCHHOFF'S LAW


Kirchoff's Current Law

states that:

The algebraic sum of the current meeting at any point in a circuit is zero

For example:
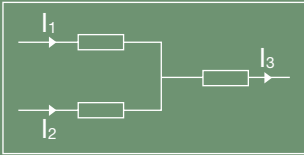
$$I_3 = I_1 + I_2 \quad \text{or} \quad I_1 + I_2 - I_3 = 0$$



(currents towards point designated as positive, those away from point negative)

In other words the sum of all currents entering a junction must equal the sum of those leaving it.

Kirchoff's Voltage Law


states that:

In travelling round any closed mesh (section) of a network (circuit), the algebraic sum of the emfs (voltages) acting in the mesh is equal to the algebraic sum of the IR voltage drops for the individual resistance in the mesh

For example:

Working anticlockwise:
 $IR_1 + IR_2 = E_1 - E_2$

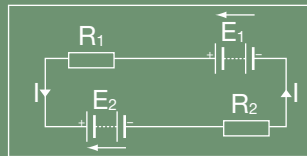Working clockwise:
 $-IR_1 - IR_2 = E_2 - E_1$



In other words the sum of all voltage sources must equal the sum of all voltages dropped across resistances in the circuit, or part of circuit.

Rapid

We bring STEAM to life

www.rapidonline.com